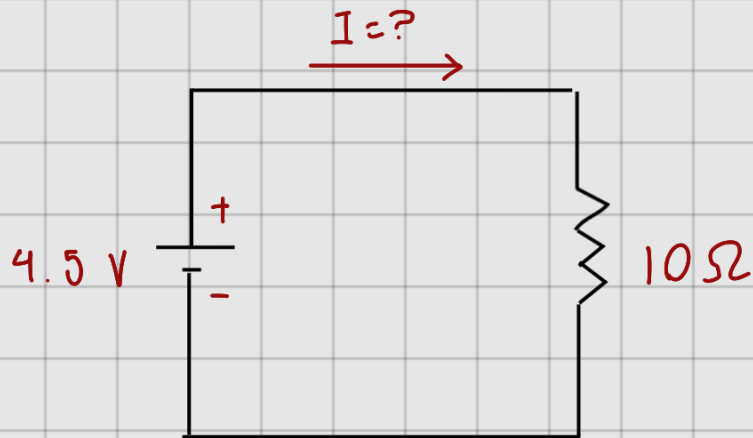


A




$$V = 4.5 \text{ V}$$

$$R = 10 \Omega$$

$$I = \frac{V}{R} = \frac{4.5 \text{ V}}{10 \Omega} = \underline{0.45 \text{ A}}$$

$$P = IV = 0.45 \text{ A}(4.5 \text{ V}) = \underline{2.025 \text{ W}}$$

B

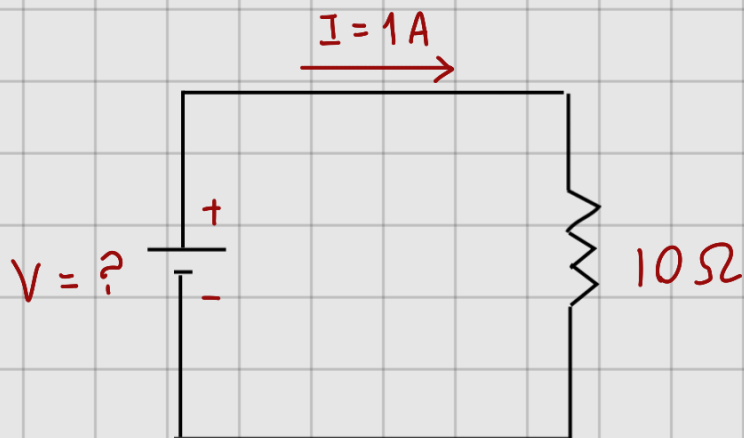


$$I = 1 \text{ A}$$

$$R = 10 \Omega$$

$$I = \frac{V}{R} \rightarrow V = IR = 1 \text{ A}(10 \Omega) = \underline{10 \text{ V}}$$

$$P = IV = 1 \text{ A}(10 \text{ V}) = \underline{10 \text{ W}}$$

C

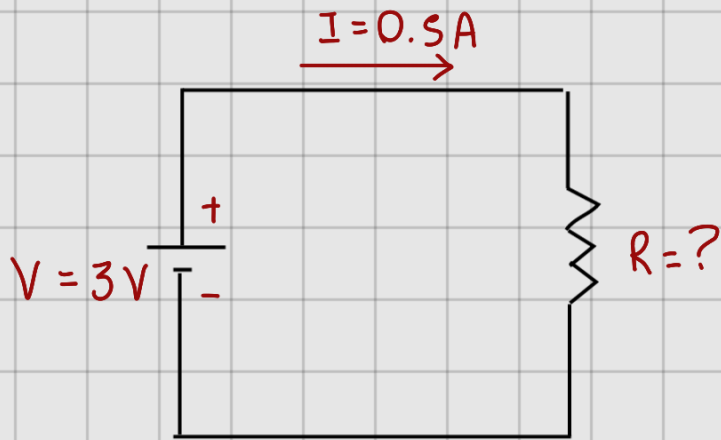


$$I = 0.5 A$$

$$V = 3V$$

$$I = \frac{V}{R} \rightarrow R = \frac{V}{I} = \frac{3V}{0.5A} = \underline{6\Omega}$$

$$P = VI = 3V(0.5A) = \underline{1.5W}$$

D

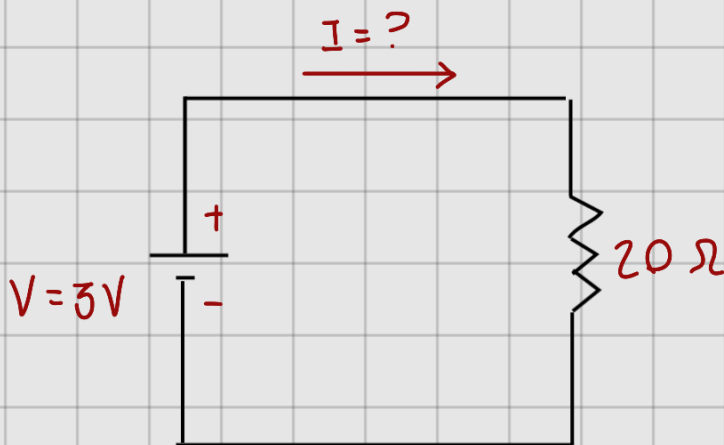


$$V = 3V$$

$$R = 20\Omega$$

$$I = \frac{V}{R} = \frac{3V}{20\Omega} = \underline{0.15A}$$

$$P = VI = 3V(0.15A) = \underline{0.45W}$$


E

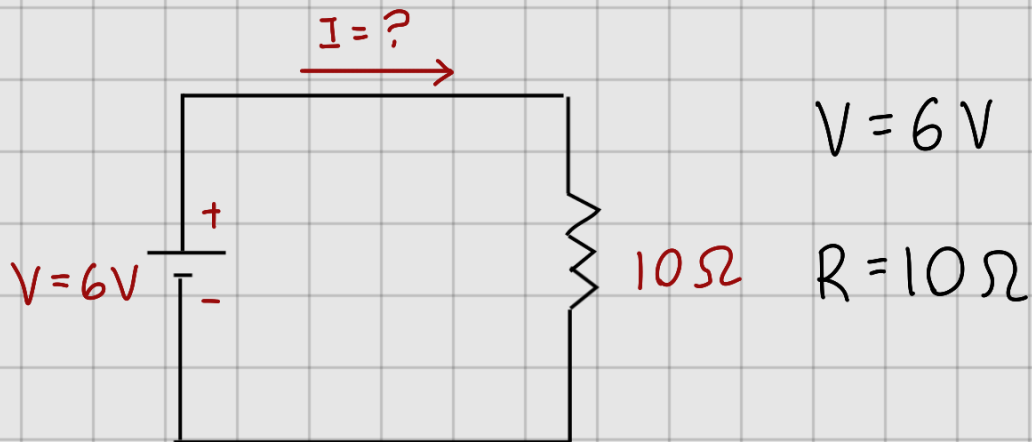

$$I = \frac{V}{R} = \frac{6V}{10\Omega} = \underline{0.6A}$$

$$P = IV = 0.6A (6V) = \underline{3.6W}$$


F

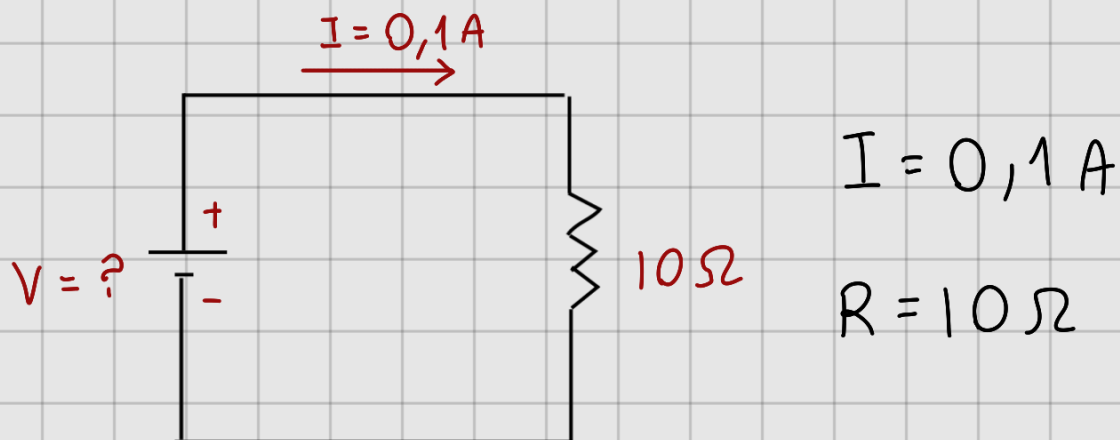

$$I = \frac{V}{R} \rightarrow V = IR = 0.1A (10\Omega) = \underline{1V}$$

$$P = IV = 0.1A (1V) = \underline{0.1W}$$


6

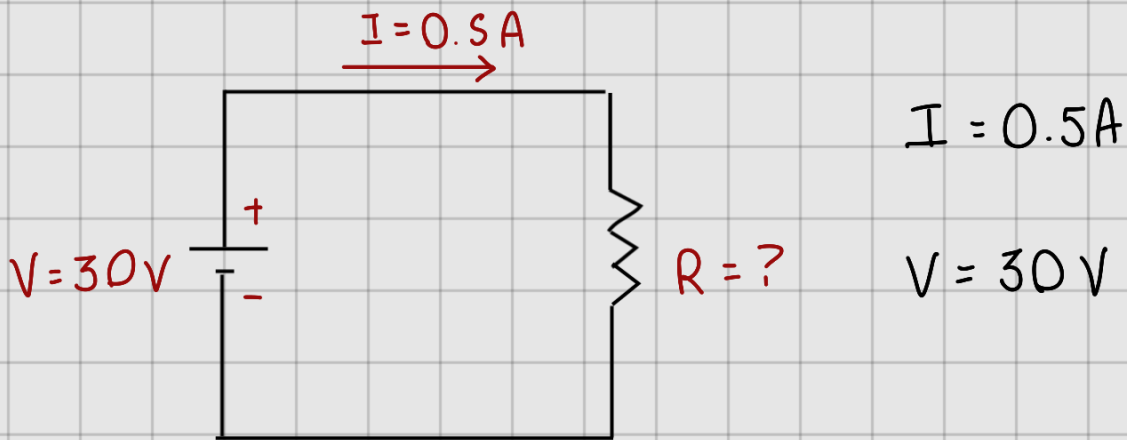

$$I = \frac{V}{R} \rightarrow R = \frac{V}{I} = \frac{30\text{V}}{0.5\text{A}} = \underline{60\Omega}$$

$$P = IV = 0.5\text{A}(30\text{V}) = \underline{15\text{W}}$$

H

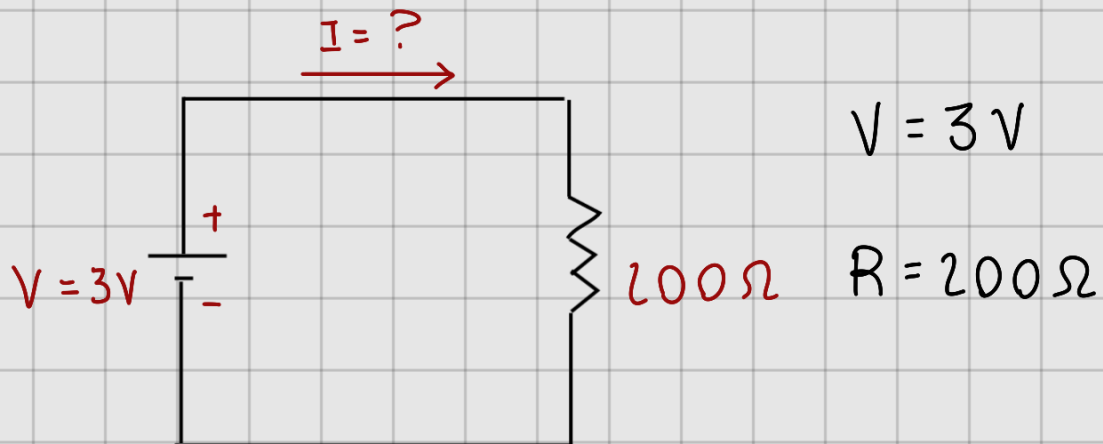

$$I = \frac{V}{R} = \frac{3\text{V}}{200\Omega} = \underline{15\text{mA}}$$

$$P = IV = 0.015\text{A}(3\text{V}) = \underline{45\text{mW}}$$