
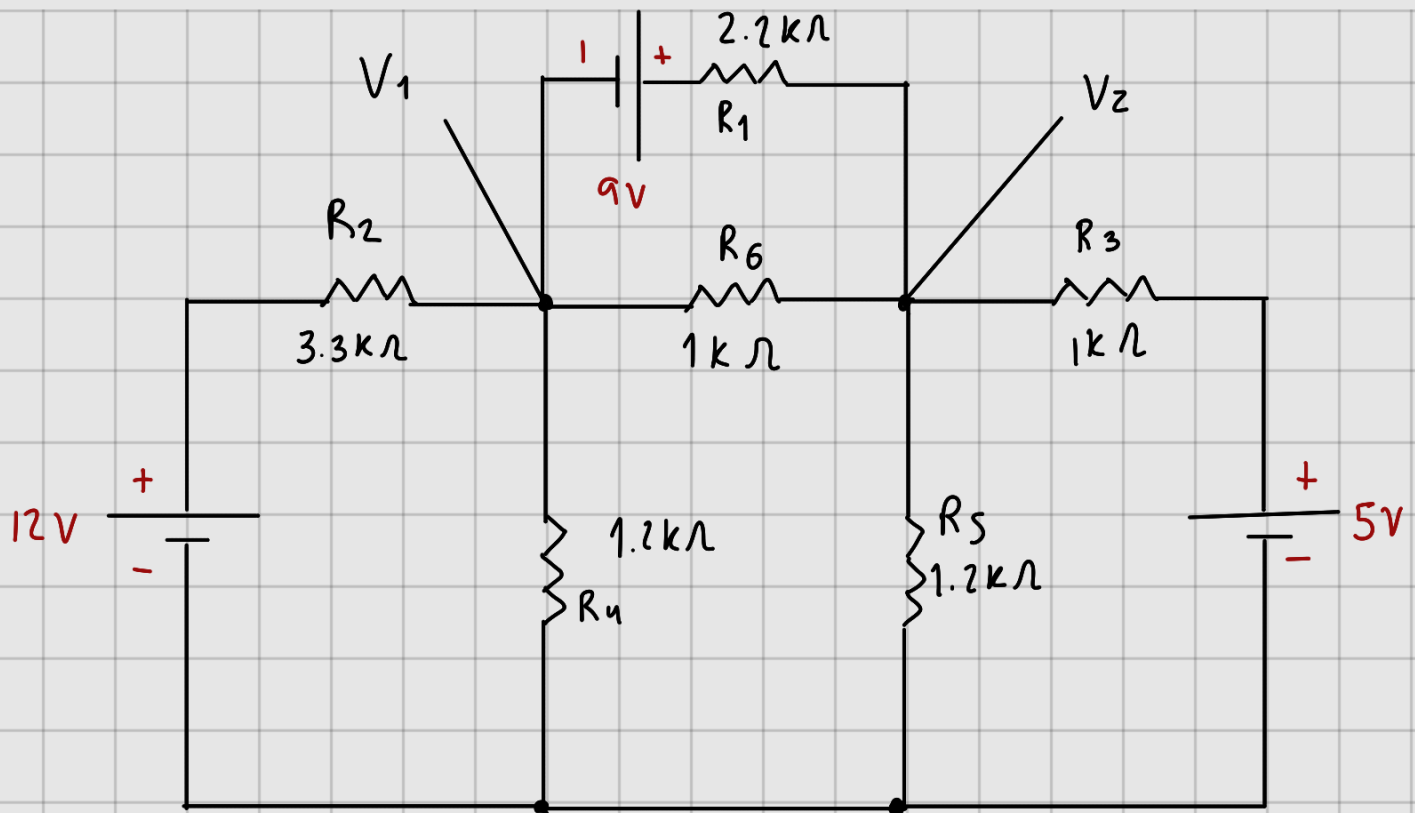


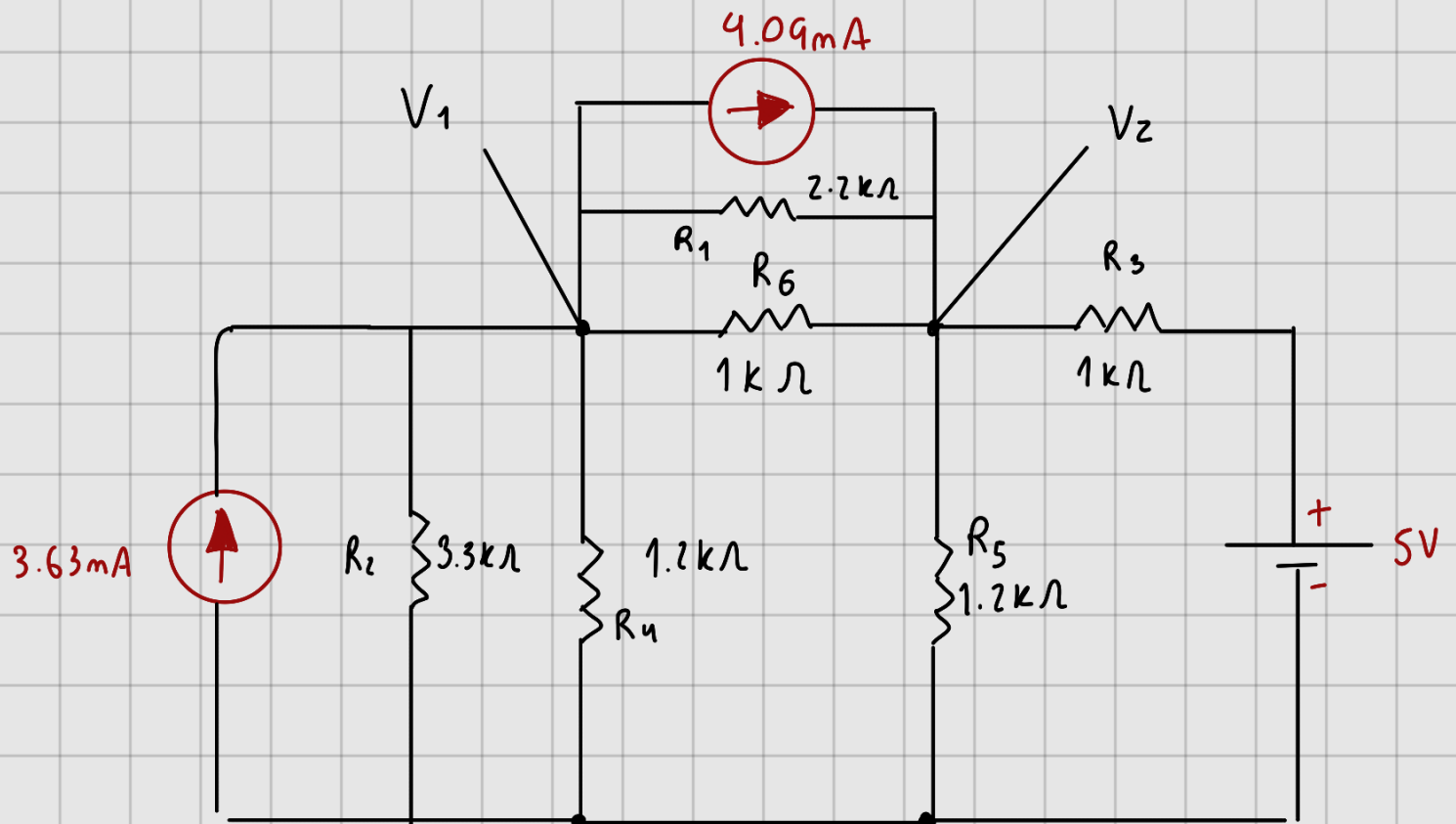


$I_{R_4}, I_{R_5}, I_{R_6}, P_{R_1}, P_{R_2}, P_{R_3}, V_1, V_2$



$$I_{S_1} = \frac{12V}{3.3k\Omega} = 3.63mA$$

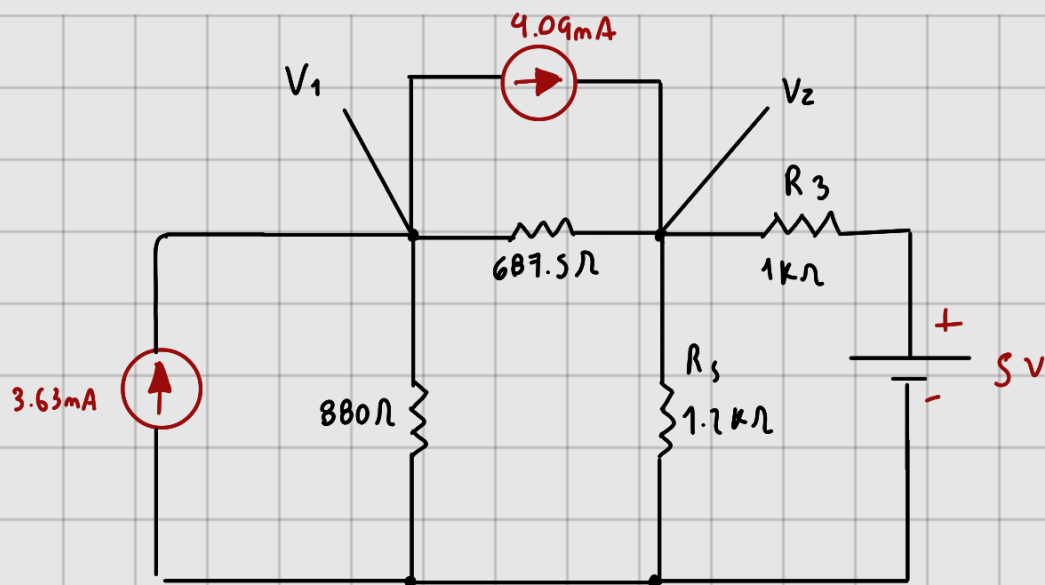
$$I_{S_3} = \frac{9V}{2.2k\Omega} = 4.09mA$$



$$R_A = \frac{1}{\frac{1}{3.3k\Omega} + \frac{1}{1.7k\Omega}} = 880\Omega$$

$$R_B = \frac{1}{\frac{1}{2.2k\Omega} + \frac{1}{1k\Omega}} = 687.5\Omega$$
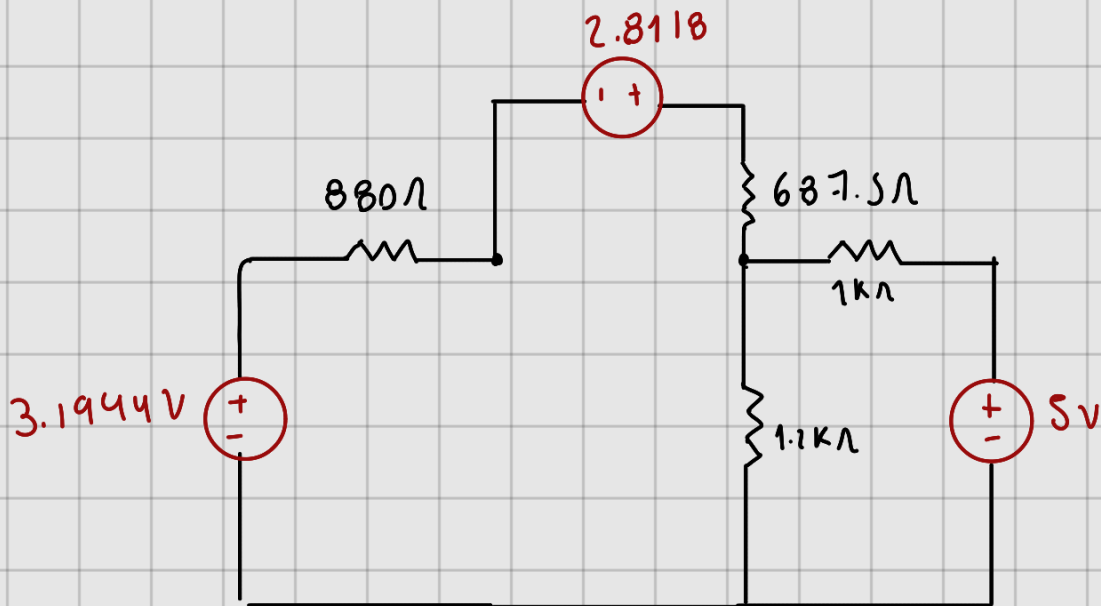
$$R_C = \frac{1}{\frac{1}{1.7k\Omega} + \frac{1}{1k\Omega}} = 545.45\Omega$$



$$V_{S_1} = 3.63mA(880) = 3.1944V$$

$$V_{S_2} = 4.09mA(687.5) = 2.8118V$$




$$R_T = 1567.5 + \frac{1}{\frac{1}{1.2k\Omega} + \frac{1}{1k\Omega}}$$

$$R_T = 2113 \Omega$$

$$I_T = \frac{6V}{2113\Omega} = 2.83mA$$

$$V = 1567.5(2.83mA)$$

$$V_1 = 1.56$$

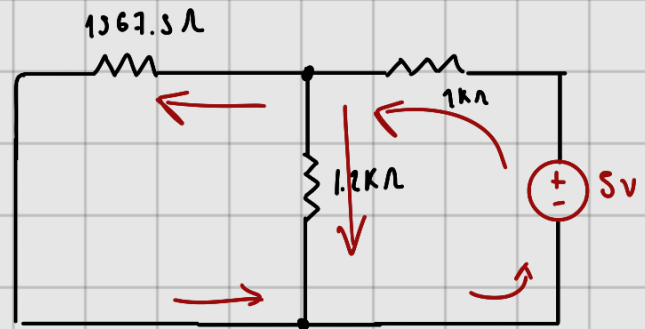

$$R_T = 1k\Omega + \frac{1}{\frac{1}{1567.5\Omega} + \frac{1}{1.2k\Omega}}$$

$$R_T = 1679.67 \Omega$$

$$I_T = \frac{5V}{1679.67} = 2.97mA$$

$$V_{1k} = 1k\Omega(2.97mA)$$

$$V_{1k} = 2.97V$$


$$V_2 = 2.03$$

$$V_2 = 2.03 + 1.56V = 3.6V$$

$$I_{R_5} = \frac{1.56}{1.2k\Omega} = 1.3mA \quad I_{R_5} = 1.6mA$$

$$I_{R_5} = 1.3mA + 1.6mA = 2.9mA$$



$$P_{R_5} = V_2 I_{R_5} = 10.44mW$$

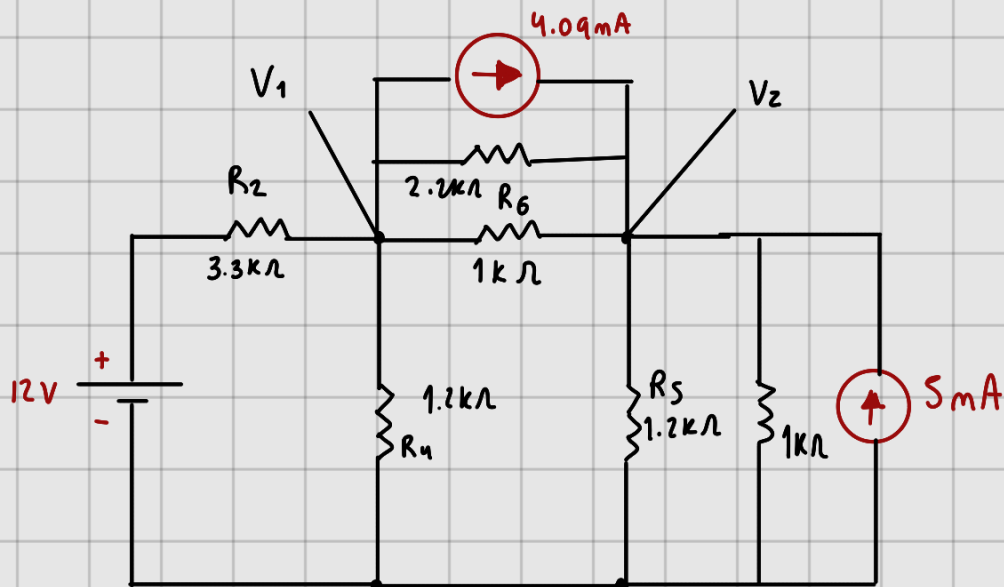

$$I_s = \frac{V_s}{R} = \frac{5V}{1k\Omega} = 5mA$$


$$R_A = \frac{1}{\frac{1}{2.2k} + \frac{1}{1k\Omega}} = 687.5\Omega$$
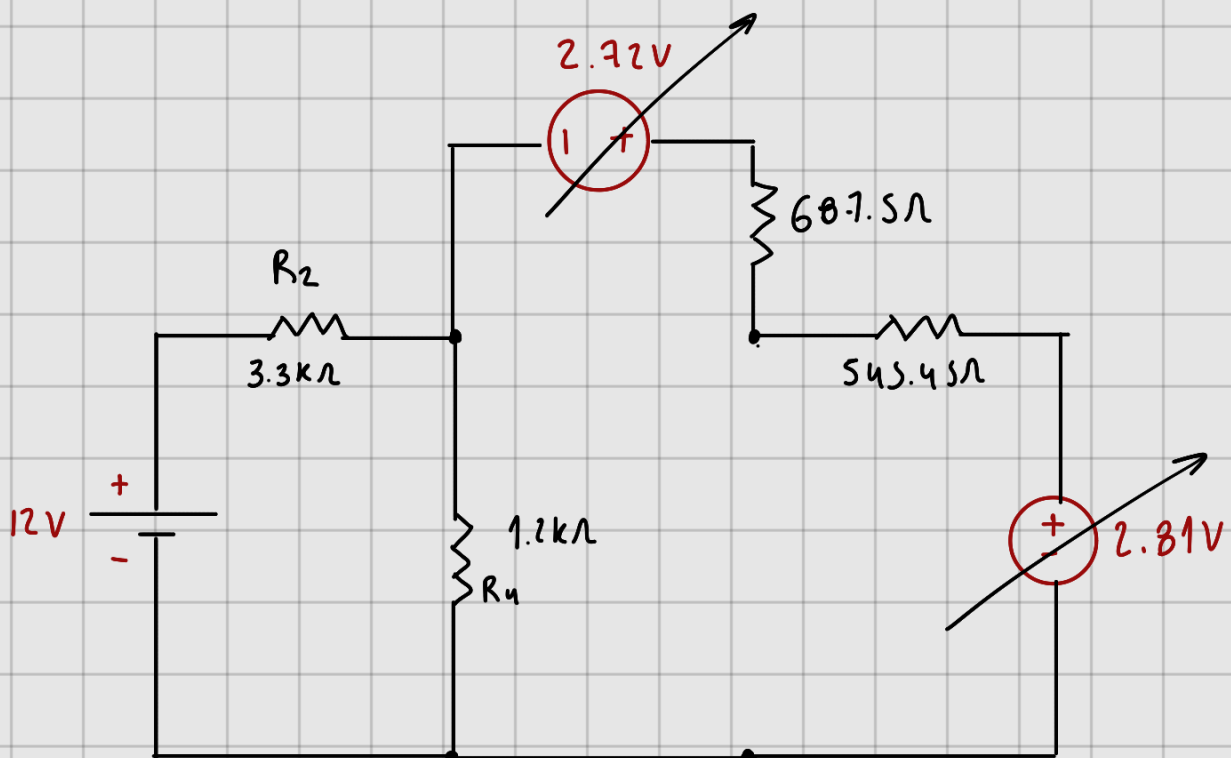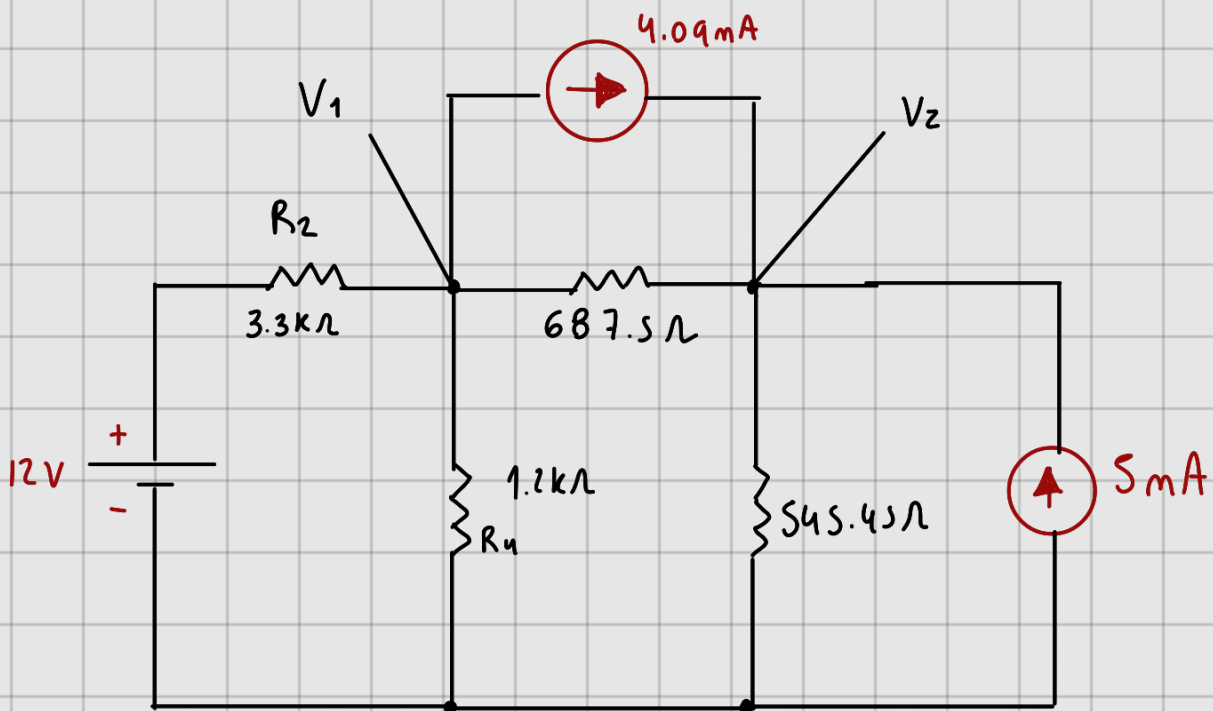
$$R_B = \frac{1}{\frac{1}{1.2k\Omega} + \frac{1}{1k\Omega}} = 545.45\Omega$$



$$V_{s_1} = 4.09 \text{ mA} (687.5 \Omega) = 2.81 \text{ V}$$
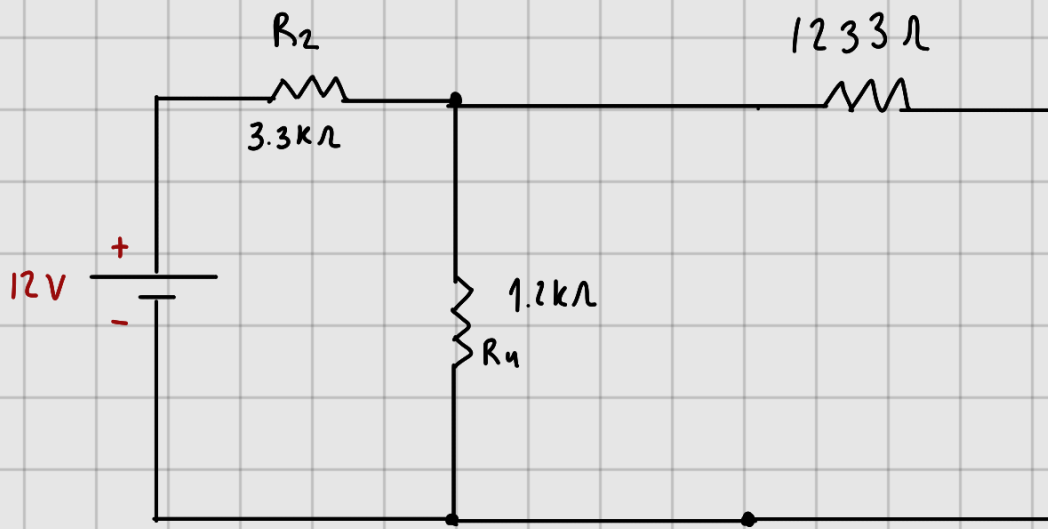
$$V_{s_2} = 5 \text{ mA} (545.45 \Omega) = 2.72 \text{ V}$$




$$R_T = 3.3\text{k}\Omega + \frac{1}{\frac{1}{1233\Omega} + \frac{1}{1200\Omega}} = 3908.1\Omega$$

$$I_T = \frac{12\text{V}}{3908.1\Omega} = 3.07\text{mA}$$

$$V_{R_2} = 10.131\text{V} \quad V_1 = 1.86\text{V}$$


$$I_{R_4} = \frac{1.86}{1200} = 1.5\text{mA}$$
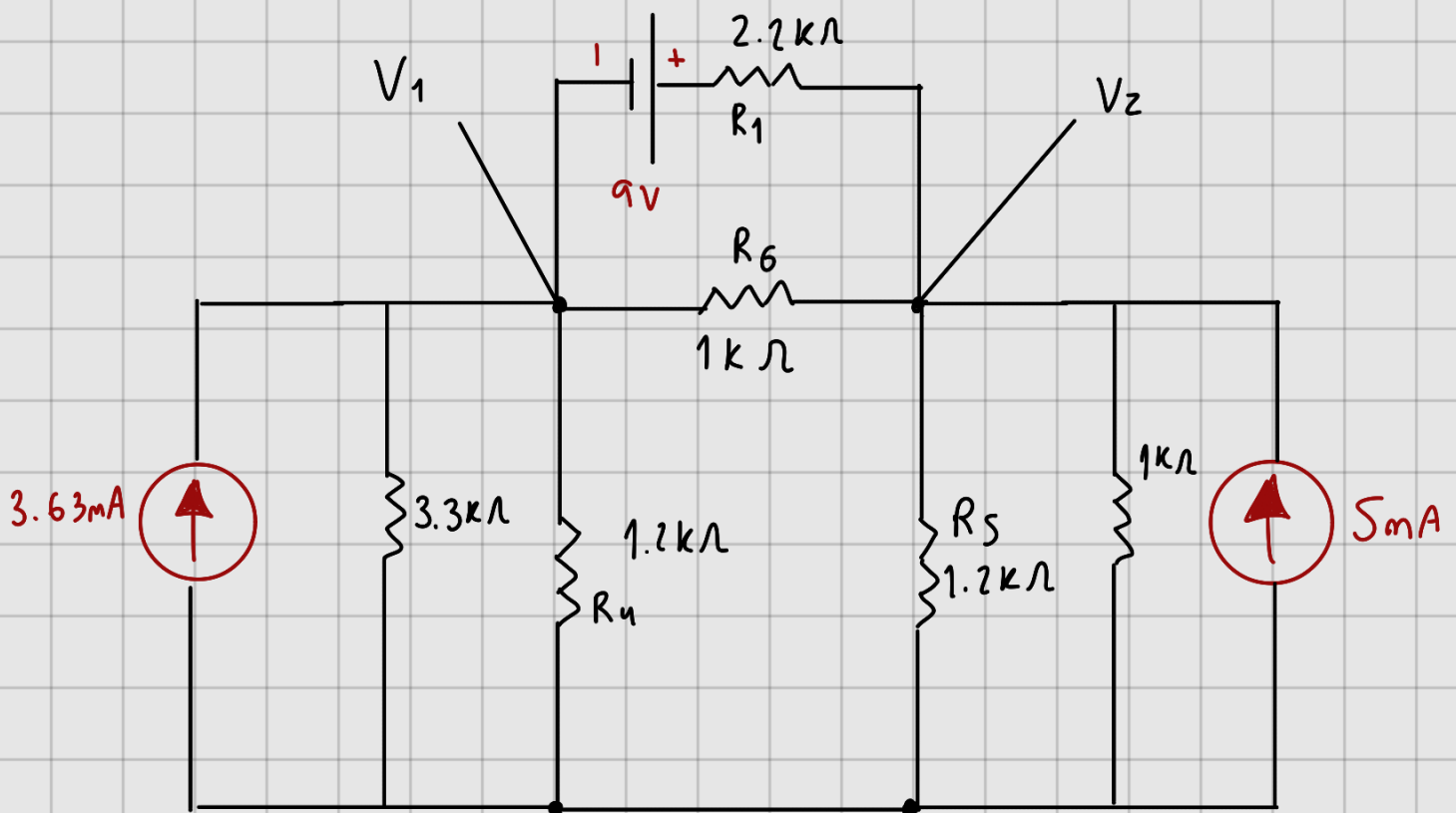
$$P_{R_4} = 1.5\text{mA}(1.86\text{V}) = 2.89\text{mW}$$



$$R_A = \frac{1}{\frac{1}{3.3k\Omega} + \frac{1}{1.2k\Omega}} = 880\Omega$$


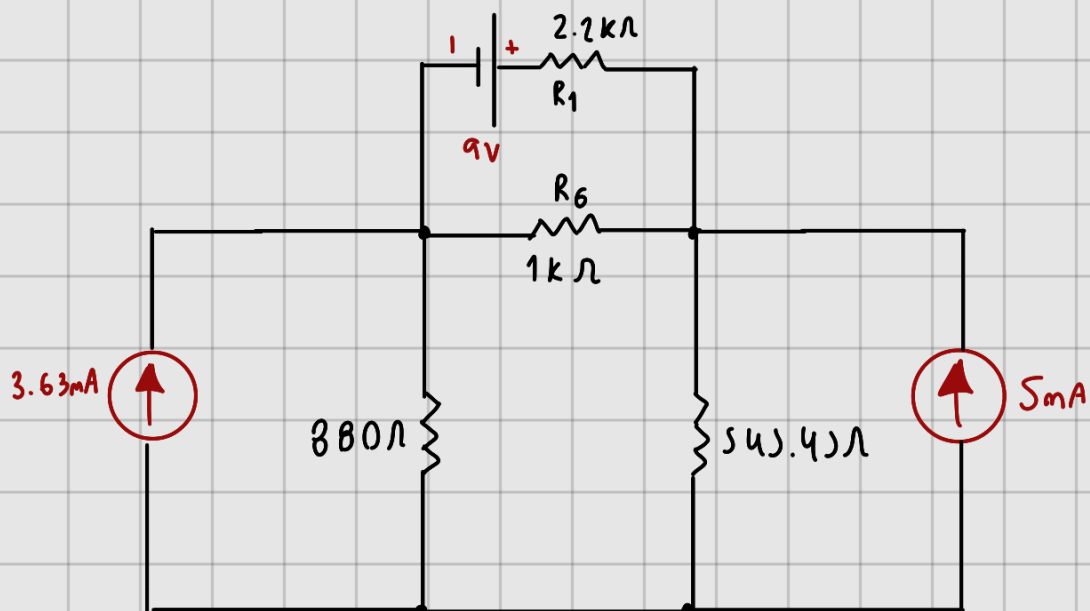
$$R_B = \frac{1}{\frac{1}{1.2k\Omega} + \frac{1}{1k\Omega}} = 545.45\Omega$$




$$V_s = 3.63 \text{ mA} (880 \Omega) \quad V_s = 5 \text{ mA} (545.45 \Omega)$$

$$V_s = 3.1944 \text{ V}$$

$$V_s = 2.7272 \text{ V}$$

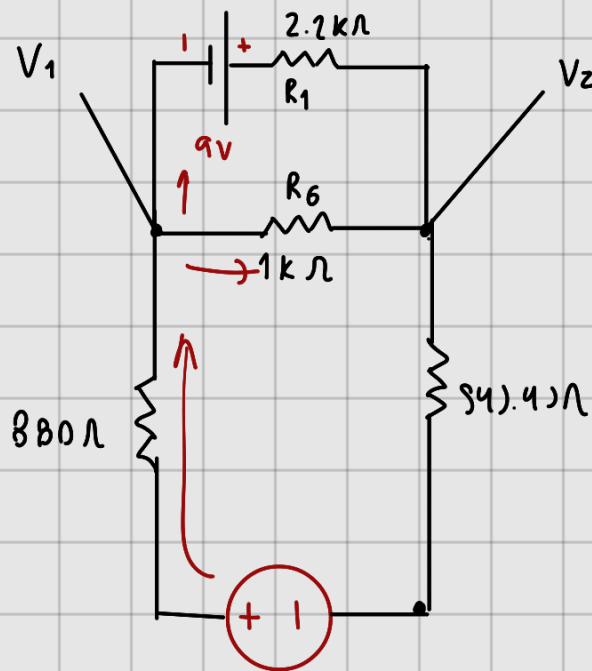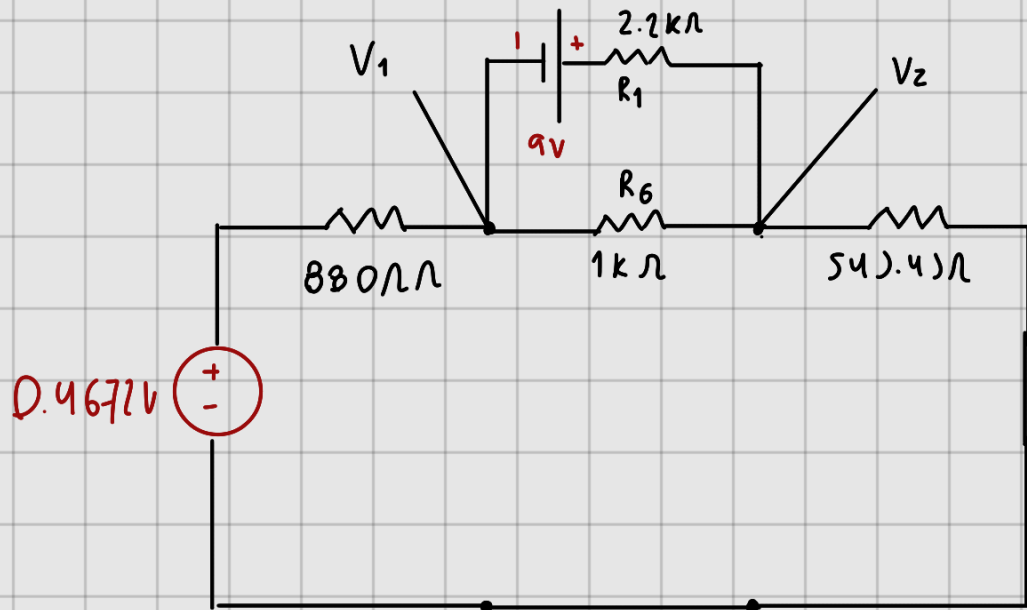

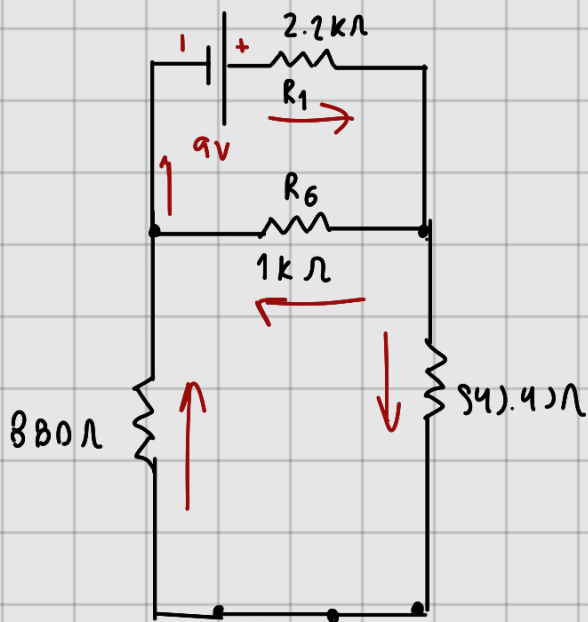

$$R_A = 1425.4 \Omega$$

$$R_T = 2787.7 \Omega$$

$$I_T = \frac{9V}{2787.7} = 3.22 \text{ mA} \quad R_T = 2113 \Omega$$

$$V_{R1} = 3.22 \text{ mA} (2.2 \text{ k}\Omega) \quad I_T = \frac{0.4672}{2113 \Omega} = 0.2 \text{ mA}$$

$$V_{R1} = 7.084 \text{ V}$$

$$V_{R1} = 880 (0.2 \text{ mA}) = 0.176 \text{ V}$$

$$V_2 = 1.916 \text{ V}$$


$$V_1 = 0.2912 \text{ V}$$

$$I_{R6} = \frac{1.916 \text{ V}}{1000 \Omega} = 1.9 \text{ mA}$$

$$I_{R6} = \frac{0.2912 \text{ V}}{1 \text{ k}} = 0.2 \text{ mA}$$

$$I_{R6} = 1.91 \text{ mA} - 0.2 \text{ mA} = 1.71 \text{ mA}$$
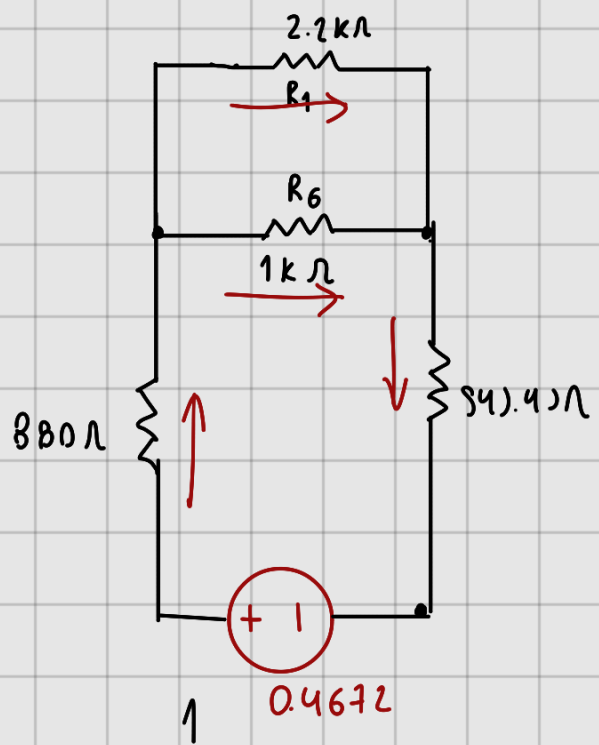
$$P_{R6} = 1.71 \text{ mA} (1.615) = 2.77 \text{ mW}$$



$$R_A = \frac{1}{\frac{1}{2.2 \text{ k}\Omega} + \frac{1}{1 \text{ k}\Omega}} = 687.5$$

$$V_1 = 1.86 \text{ V}$$

$$V_2 = 3.6 \text{ V}$$

$$I_{R_4} = 1.5 \text{ mA}$$

$$I_{R_5} = 2.9 \text{ mA}$$

$$I_{R_6} = 1.71 \text{ mA}$$

$$P_{R_4} = 2.89 \text{ mW}$$

$$P_{R_5} = 10.44 \text{ mW}$$

$$P_{R_6} = 2.77 \text{ mW}$$