

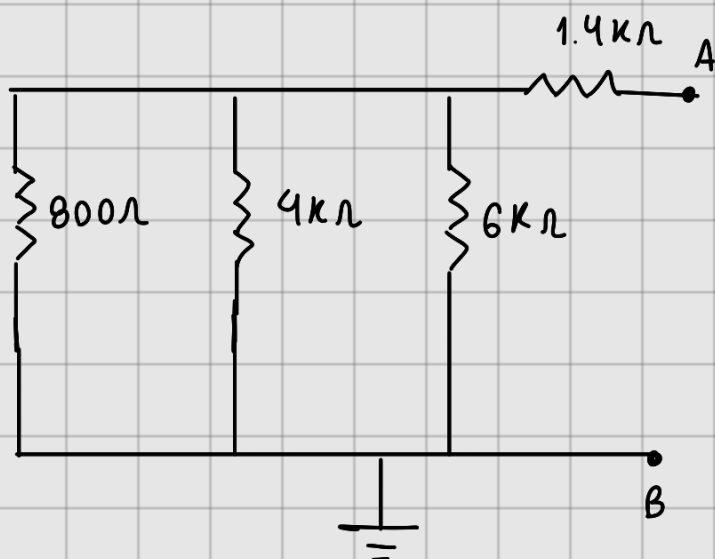


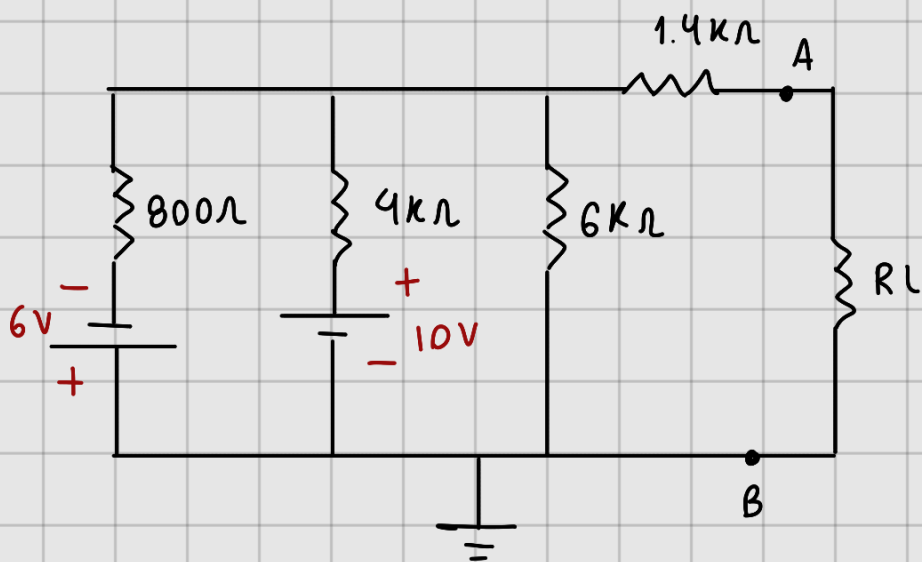


$$R_A = \frac{1}{\frac{1}{800\Omega} + \frac{1}{4k\Omega} + \frac{1}{6k\Omega}}$$

$$+ 1.4k\Omega = 2k\Omega$$

$$R_{TH} = 2k\Omega$$

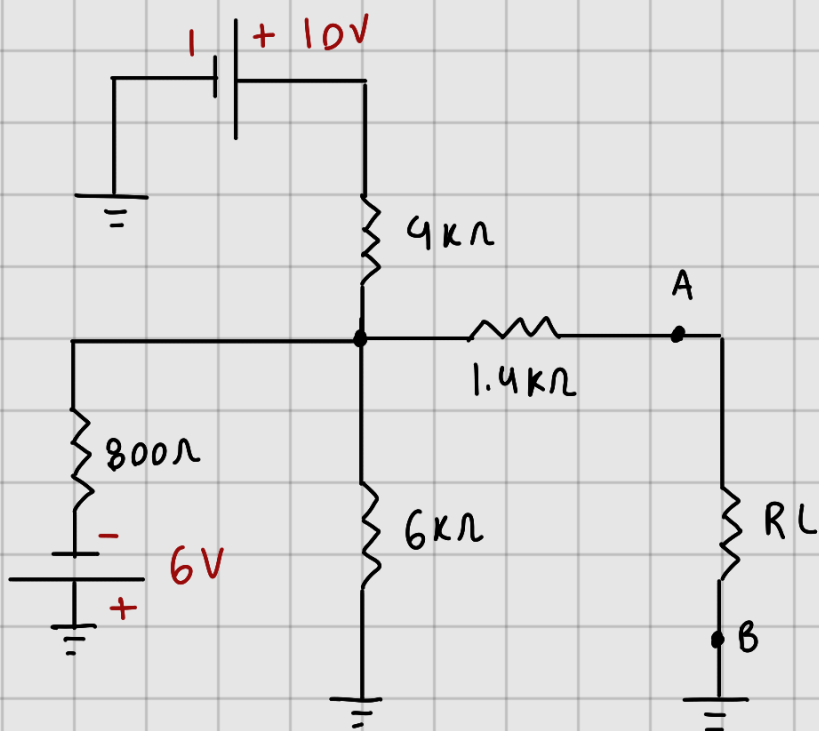


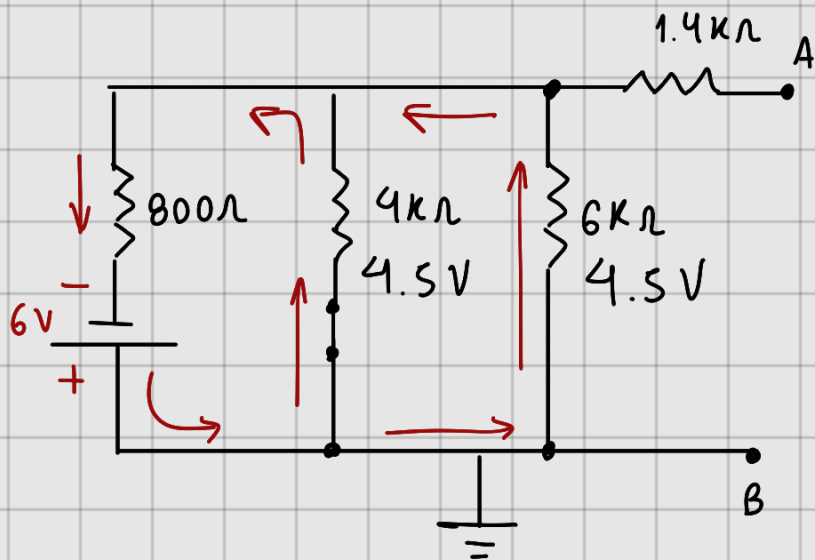

$$R_T = 3.2k\Omega$$

$$I = \frac{V}{R_T} = \frac{6V}{3.2k\Omega} = 1.875mA$$

$$V_{TH} = 4.5V$$

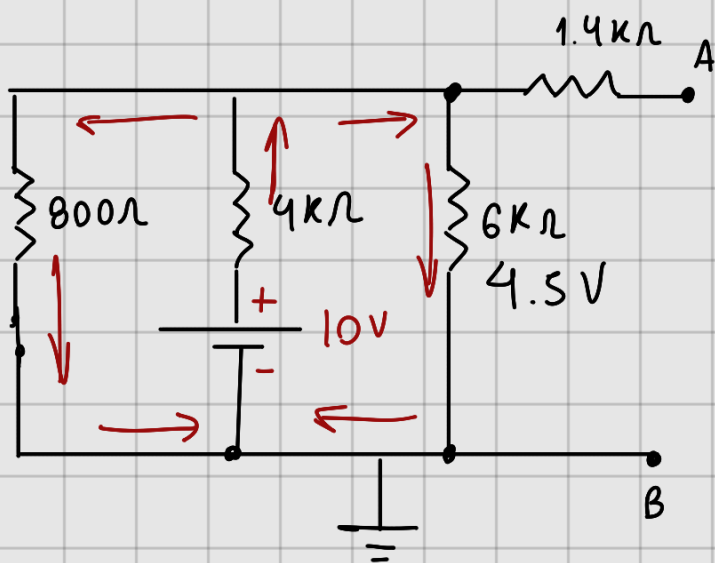

$$R_T = 4705.88\Omega \quad I_T = \frac{10V}{4705.88\Omega} = 2.125mA$$



$$V_{4k\Omega} = 2.125mA (4k\Omega) = 8.5V$$

$$V_{TH}' = 1.5 V$$


$$V_{TH} = 4.5 V + 1.5 V = 6 V$$

$$V_{TH} = 6 V$$

$$R_{TH} = 2 k\Omega$$

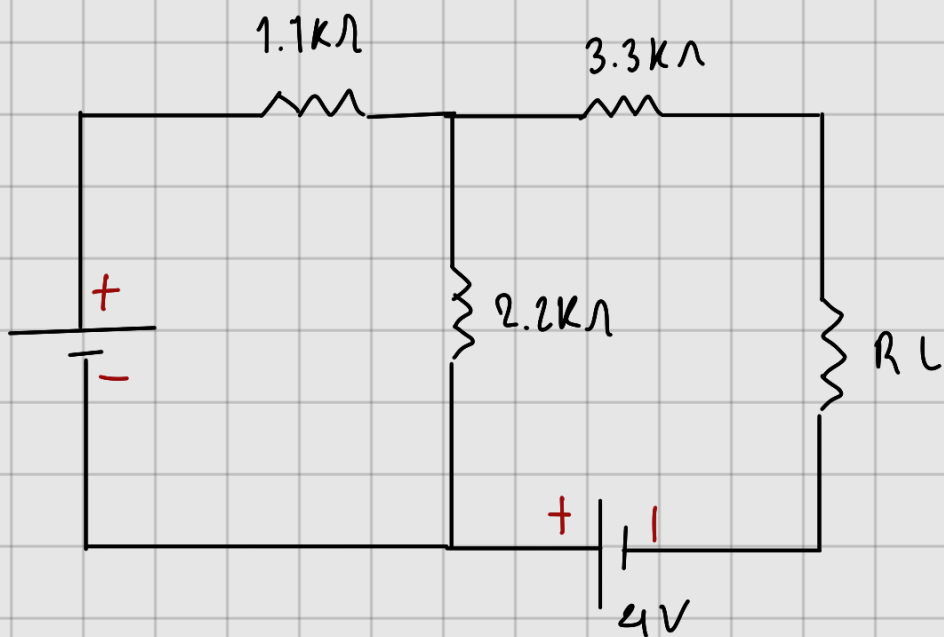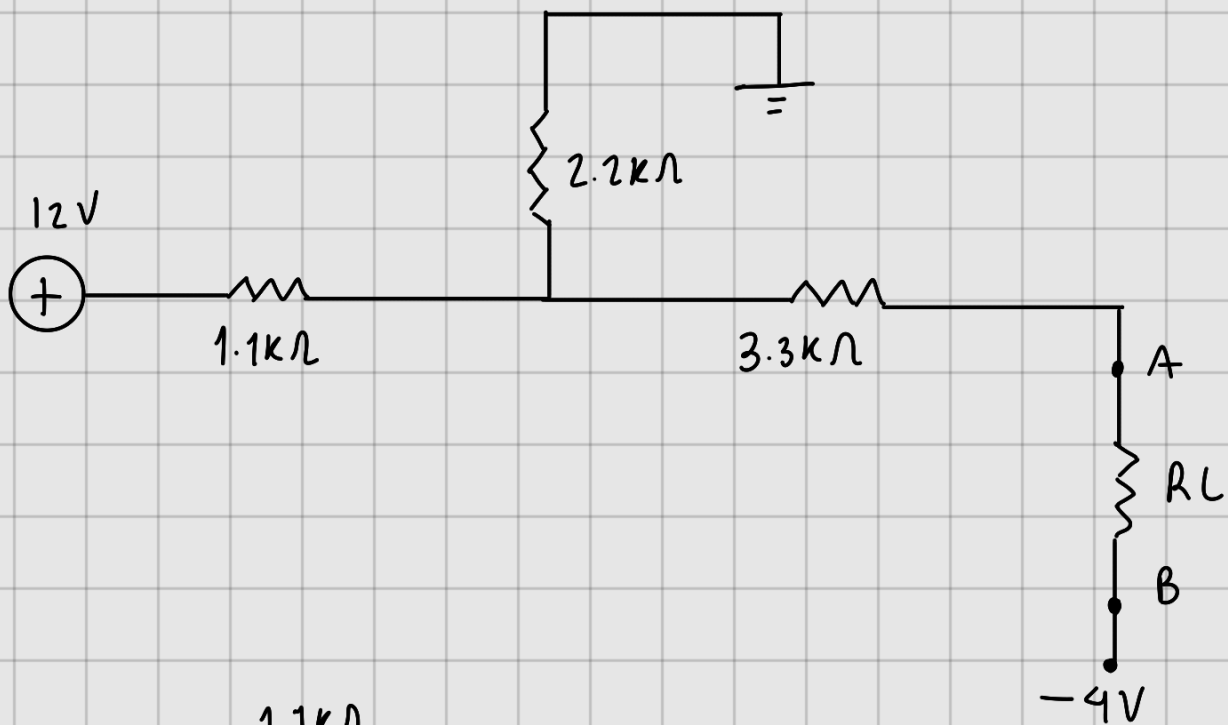

$$R_{TH} = 4033.33\Omega$$

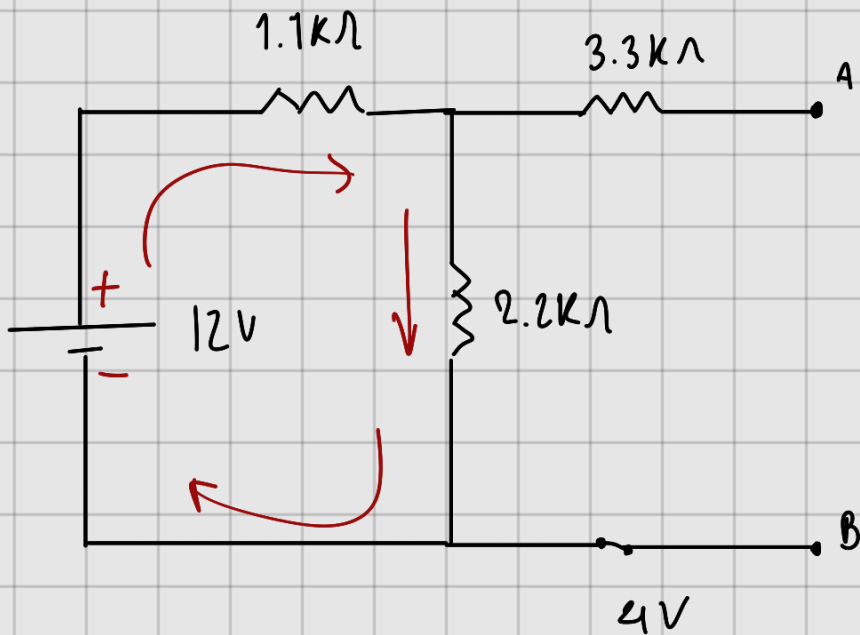


$$R_T = 3.3 \text{ k}\Omega$$

$$I = \frac{12 \text{ V}}{3.3 \text{ k}\Omega} = 3.63 \text{ mA}$$

$$V_{1.1 \text{ k}\Omega} = IR = 3.63 \text{ mA} (1.1 \text{ k}\Omega) = 4 \text{ V}$$

$$V_{2.2 \text{ k}\Omega} = 12 \text{ V} - 4 \text{ V} = 8 \text{ V}$$

$$V_{TH} = 8 \text{ V}$$

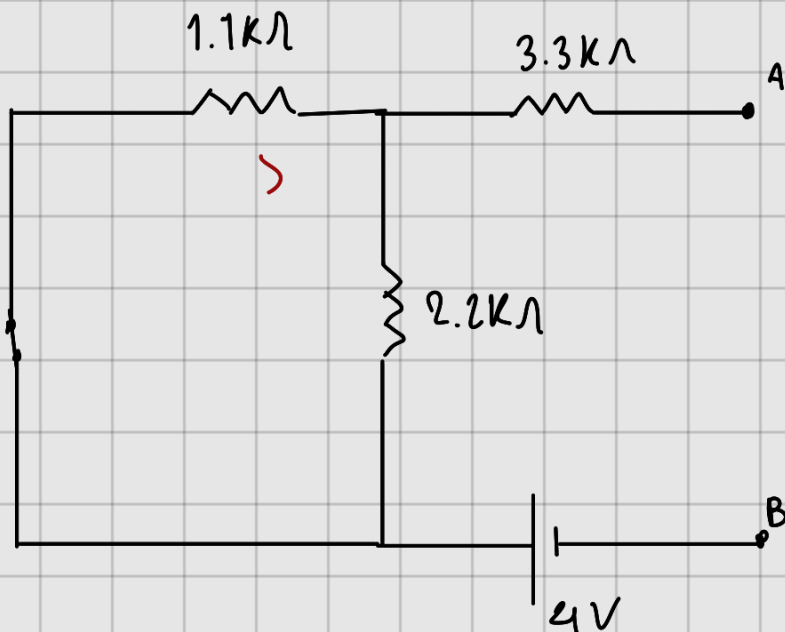

$$V_{TH} = 4 \text{ V}$$

$$V_{TH} = 8 \text{ V} + 4 \text{ V}$$

$$\underline{V_{TH} = 12 \text{ V}}$$