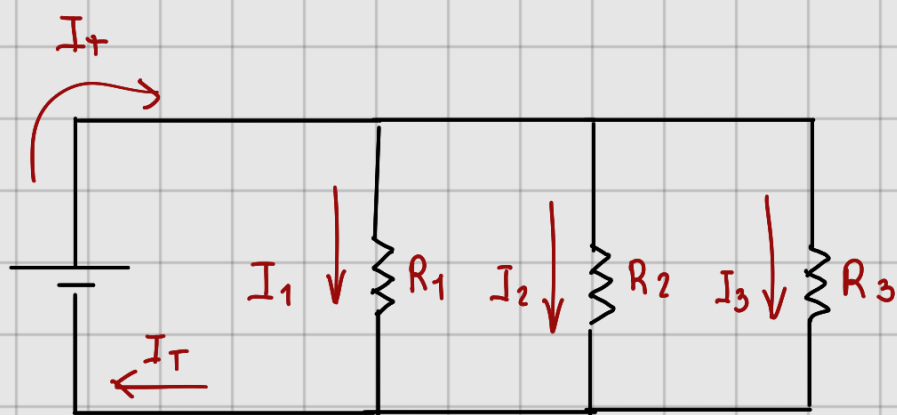




$$I_T = 100 \text{ mA}$$

$$I_1 = 30 \text{ mA}$$

$$I_2 = 50 \text{ mA}$$

$$I_3 = 20 \text{ mA}$$

$$I_T - I_1 - I_2 - I_3 = 0$$

$$100 \text{ mA} - 30 \text{ mA} - I_2 - 20 \text{ mA} = 0$$

$$50 \text{ mA} - I_2 = 0$$

$$I_2 = 50 \text{ mA}$$

$$R_1 = 1 \text{ k}\Omega$$

$$V_T = I_1 R_1 = 30 \text{ mA} (1 \text{ k}\Omega)$$

$$R_2 = ?$$

$$= 30 \text{ V}$$

$$R_3 = ?$$

$$R_2 = \frac{V_T}{I_2} = \frac{30}{50 \text{ mA}} = 600 \Omega$$

$$R_T = ?$$

$$R_3 = \frac{V_T}{I_3} = \frac{30}{20 \text{ mA}} = 1.5 \text{ k}\Omega$$

$$V = ?$$

$$R_T = \frac{1}{1/600 + 1/1500 + 1/1000} = \frac{1}{3.333 \text{ m}\Omega} = 300 \Omega$$

$$I_T - I_1 - I_2 - I_3 = 0$$

$$\frac{V_T}{R_T} - \frac{V_T}{R_1} - \frac{V_T}{R_2} - \frac{V_T}{R_3} = 0$$

$$\frac{30}{300} - \frac{30}{1000} - \frac{30}{600} - \frac{30}{1500} = 0$$

$$100\text{mA} - 30\text{mA} - 50\text{mA} - 20\text{mA} = 0$$

$$R_1 = 1\text{K}\Omega$$

$$R_2 = 600\Omega$$

$$R_3 = 1.5\text{K}\Omega$$

$$R_T = 300\Omega$$

$$V = 30\text{V}$$
