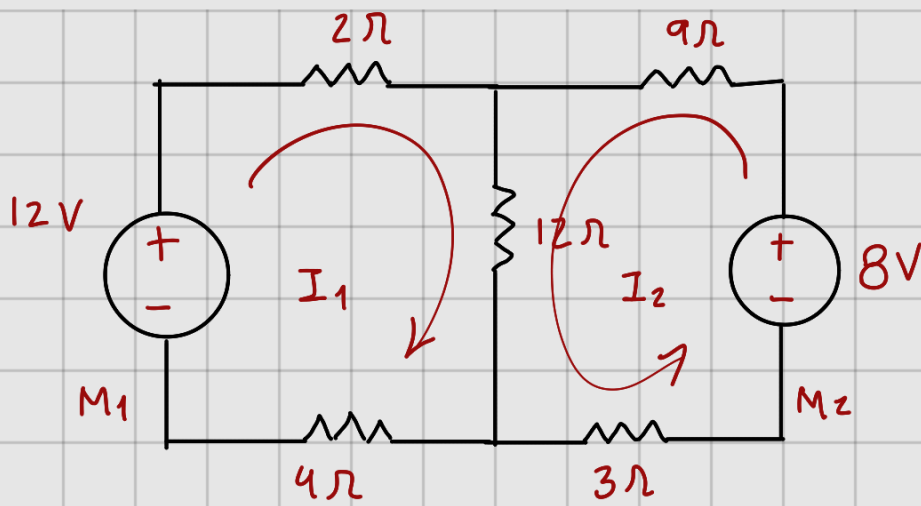




$$M_1) \quad 2\Omega i_1 + 12\Omega (i_1 + i_2) + 4\Omega i_1 = 12V$$

$$2\Omega i_1 + 12\Omega i_1 + 12\Omega i_2 + 4\Omega i_1 = 12V$$

$$18\Omega i_1 + 12\Omega i_2 = 12V$$

$$M_2) = 9\Omega i_2 + 3\Omega i_2 + 12\Omega (i_2 + i_1) = 8V$$

$$9\Omega i_2 + 3\Omega i_2 + 12\Omega i_2 + 12\Omega i_1 = 8V$$

$$24\Omega i_2 + 12\Omega i_1 = 8V$$


$$18\Omega i_1 + 12\Omega i_2 = 12V$$

$$12\Omega i_2 + 24\Omega i_2 = 8V$$

$$18\Omega i_1 - 12\Omega i_2 = 12V$$

$$i_1 = 0.666 A$$

$$i_2 = 0$$

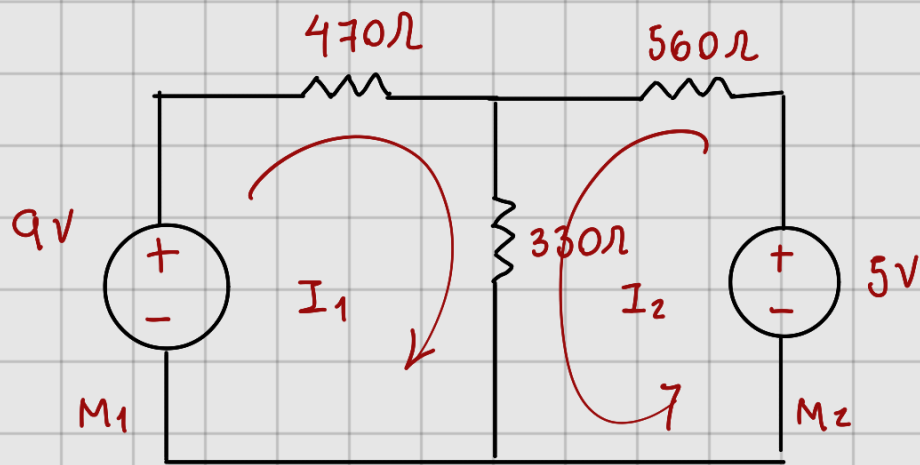

$$470i_1 + 330(i_1 + i_2) = 9V$$

$$470i_1 + 330i_1 + 330i_2 = 9V$$

$$800i_1 + 330i_2 = 9V$$

$$560i_2 + 330(i_2 + i_1) = 5V$$

$$560i_2 + 330i_2 + 330i_1 = 5V$$

$$890i_2 + 330i_1 = 5V$$

$$800i_1 + 330i_2 = 9V$$

$$330i_1 + 890i_2 = 5V$$

$$i_1 = 10.5mA$$

$$i_2 = 1.7mA$$