

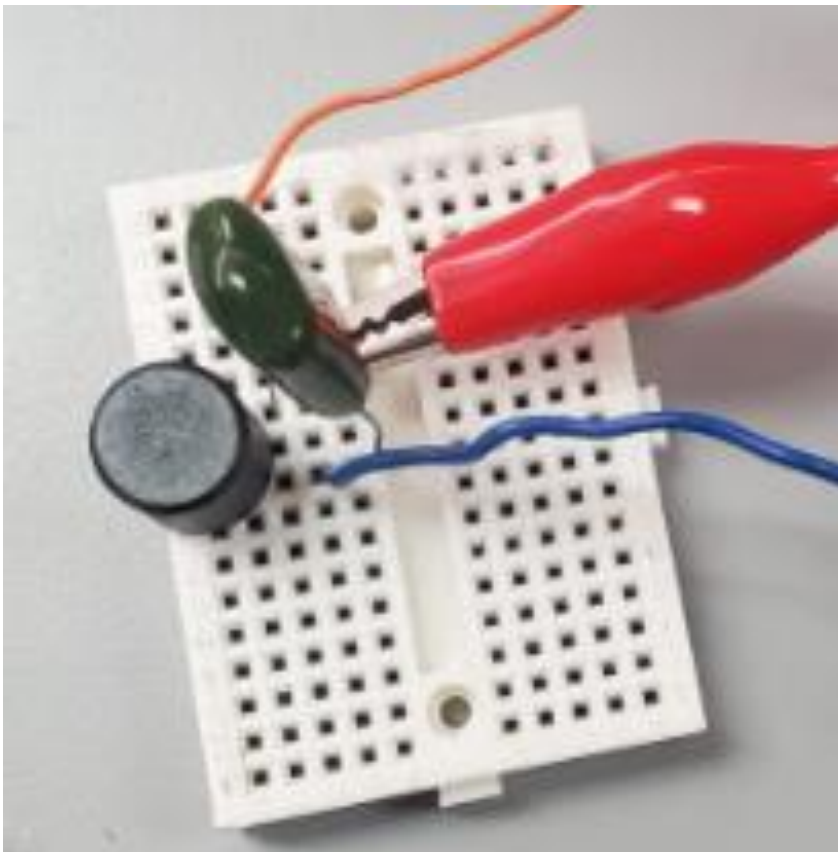


PRACTICA CIRCUITO LC

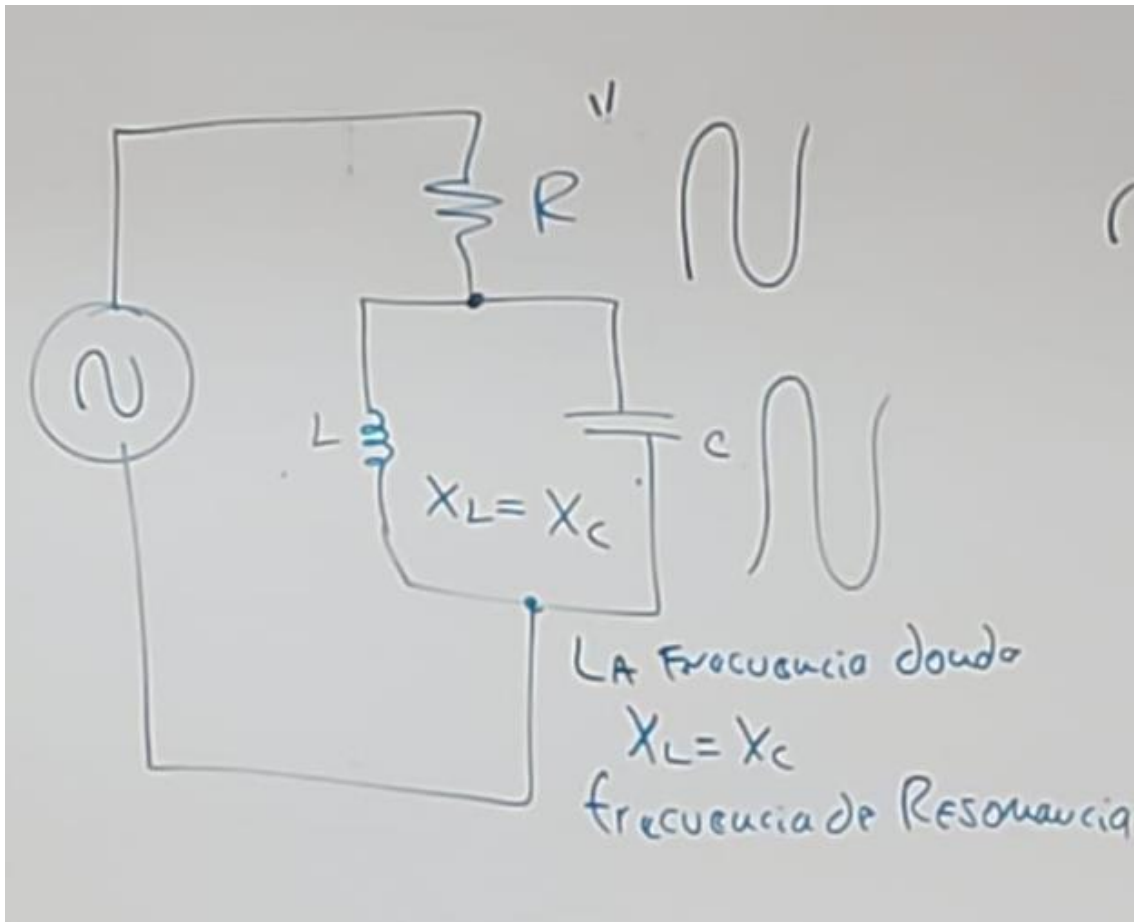

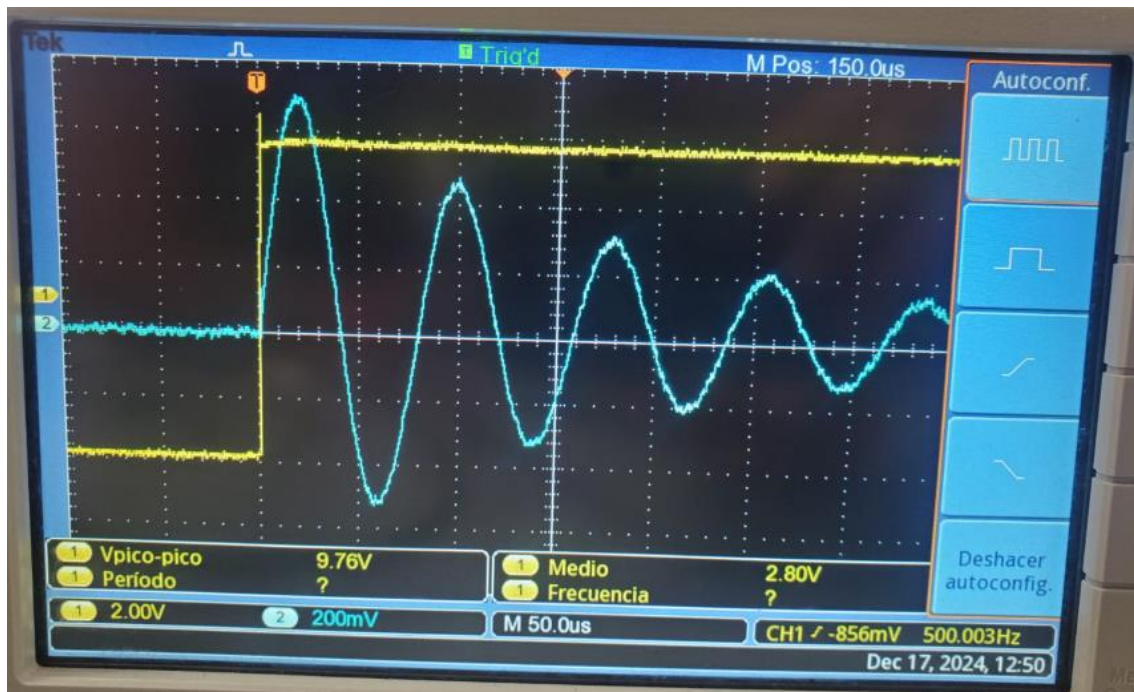


$P=80\mu s$

$F=1/P=1/80\mu s = 12.5\text{ kHz}$ es igual a la frecuencia de resonancia


-2k Hz	-1k Hz	-1 K Hz	F resonancia	+1 k Hz	+1 K Hz	+2 K Hz
720 mVpp	1.4 Vpp	3.56 Vpp	5.6 Vpp	4 Vpp	2.58 Vpp	1.22 Vpp

Frecuencia de resonancia

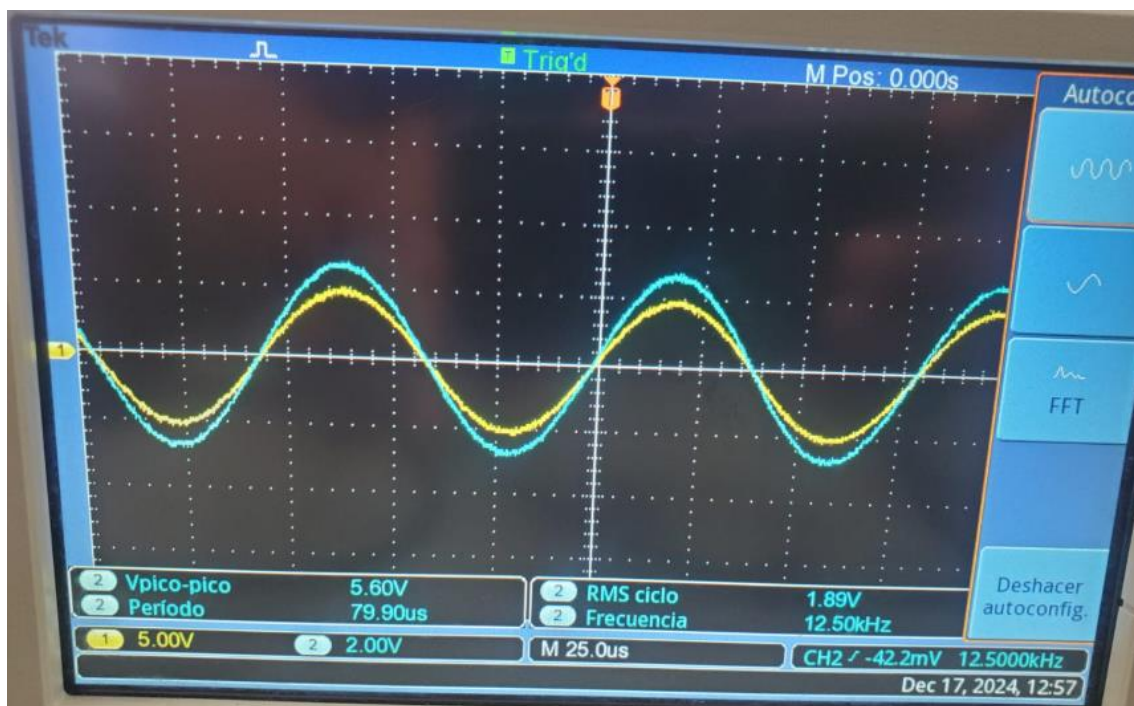



+1 K hz= 13.5 K hz

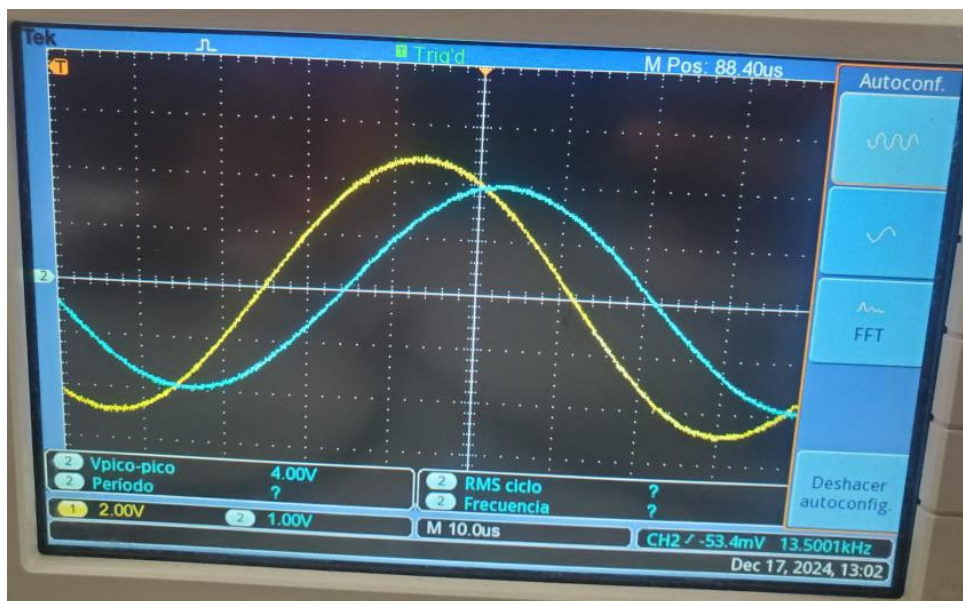

-1KHz = 11.5 KHz

